

Lessons Learned from Power Integrity

presented by:
Charles Hymowitz of AEi Systems

© AEi Systems 2018

ae systems
ANALYTICAL HEAVY LIFTING

PI is Not My Problem

“Power is not my problem, its yours.”

-- high speed designer

“What do you want, I gave you 5Vdc?!?!”

-- power supply designer

Dirty Secret: They're both wrong.

Power is everyone's problem.




Power Supply Designers
& Manufacturers

PCB
Designers

Circuit Designers


Power Integrity Applies to Everyone

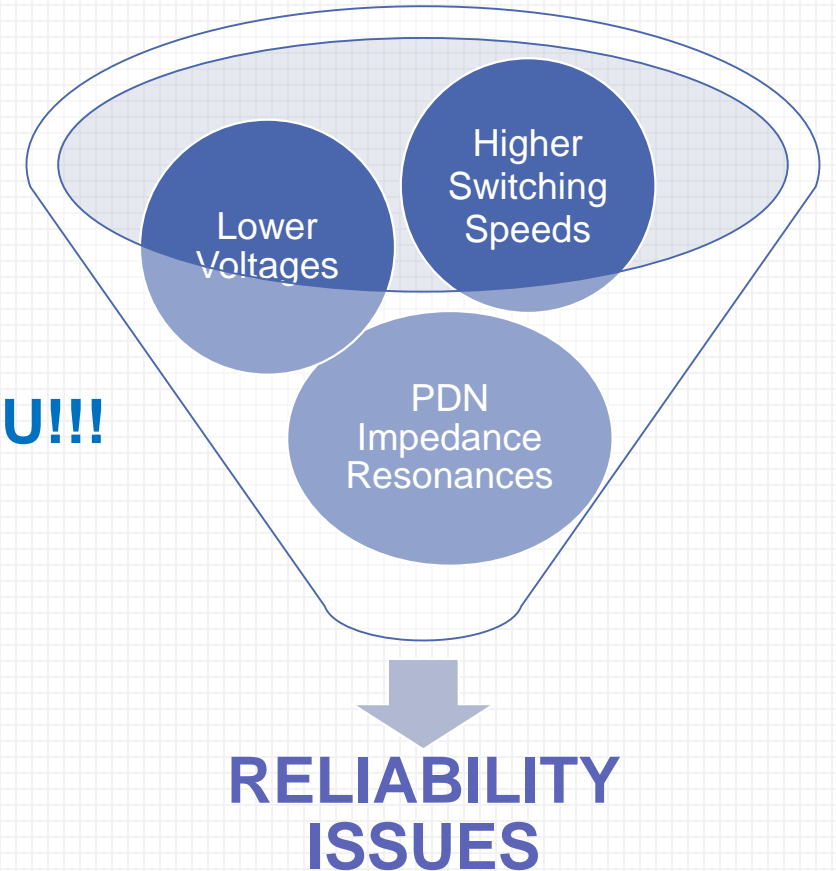- Power Integrity is about getting the right power to the load
- PI is NOT A SYSTEM ISSUE!
- PI is NOT A HIGH-SPEED ISSUE!
- PI is NOT A POWER SUPPLY ISSUE!
- It is an **EVERYONE** issue - YES, IT APPLIES TO YOU!!!
- Overstress and regulation issues? Sure.
- Dynamic current issues? Sure.
- Low current issues? Sure.
- Jitter issues? Sure.
- Heritage design issues? Sure.



"The Unfortunate State of Power Integrity in Space Systems" – Space Power Workshop 2017


The Power Distribution Network (PDN)

 

What we get


What we want

Planes


 


Power Integrity is about controlling FLAT impedance

 The Basic Problem: How we get into trouble




But this what we build!

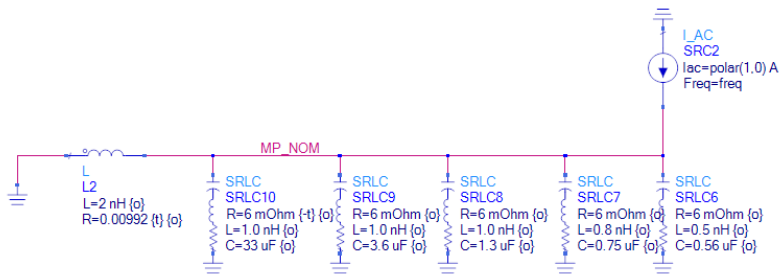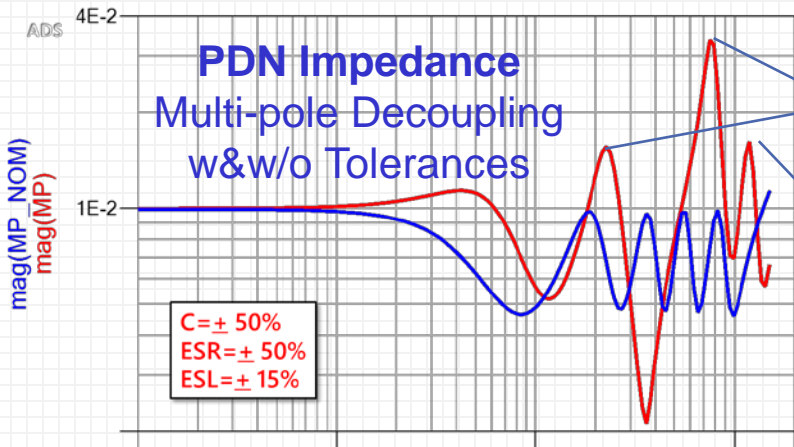

Poor Power Integrity Design

This is the spec

 

DC + Ripple + CS + SL + Noise < 5% of Vsup

Fighting a Lack of Data

- **These things are impacting designs and they need to be considered and addressed**
- **Impedance is how we communicate – it's the answer**
 - ❖ IC manufacturers need to provide the output impedance data
 - ❖ VRM Models need to reflect accurate output impedance and they usually don't - RL models are a minimum
 - ❖ Capacitor models are often bandwidth limited and not measured using a 2-port measurement
- **Impedance needs to be Flat**
 - ❖ There's a VRM, a plane, and a load. How do we make them like each other?
 - ❖ You can't pick a VRM because of its size **pick it for its impedance**
 - ❖ Decoupling needs to be appropriate for the dynamic currents **and is specific to a PCB design**
- **Lack of Awareness The power supply is a common source of system issues**
 - ❖ Poor EVMs, Reference Designs, and Lack of Trade Studies **result in system issues**
 - ❖ Parts and EDUs often not available for testing before the final design pass **EM is Simulation needed**
 - ❖ Where are the resonances, what are the dynamic currents?
 - ❖ You almost always need an iteration

**It's easy to get right if you follow a few basic rules and
Measure - Model - Simulate - Measure**

Example: Power to Core WCCA

■ The Target Impedance Concept

Each power rail has an allowed voltage range to work with, often 5% of V_{out} , but can be smaller or larger. For example, a 2.5V power source supplying 1A, may have an allowed operating range of 5%...

$$\Delta V = 2.5V \cdot 5\% = \pm 125mV$$

From this allowed range, subtract the DC terms, ripple and PSRR to determine the Target Impedance. Some engineers BUDGET 1/3rd of the noise for dynamic current, which would reduce this to $\pm 42mV$. Sensitive circuits that include PLLs, such as SERDES transceivers are often lower voltage and typically $\pm 20mV$ or less.


Assuming one resonant peak and excitation at the resonant peak frequency

$$BW(Trise) = \frac{0.35}{Trise}$$

$$Z_{Target} = \frac{(Power_Supply_Voltage) \times (Allowed_Ripple)}{Current}$$

$$+2.5V_Target_Impedance = \frac{1}{3} \cdot \frac{2.5V \cdot 5\%}{1A \cdot 50\%} = 0.083\Omega$$




 
While the edge speed and dynamic current are unknown, a conservative BW limit was 300MHz in this case





Example: Power to Core WCCA

- Compliance: $Q < 2$ and Impedance $< 0.083\Omega$



Improper capacitor selection

   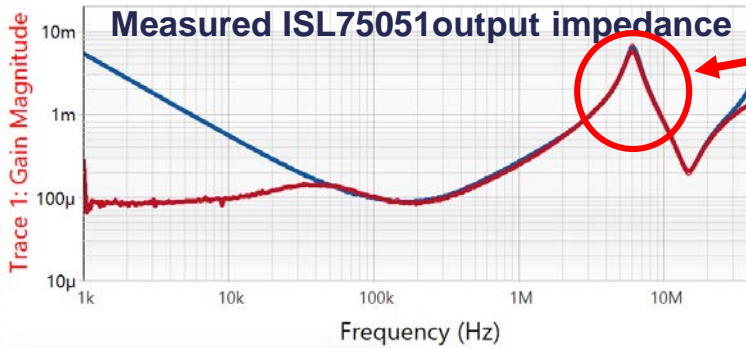

 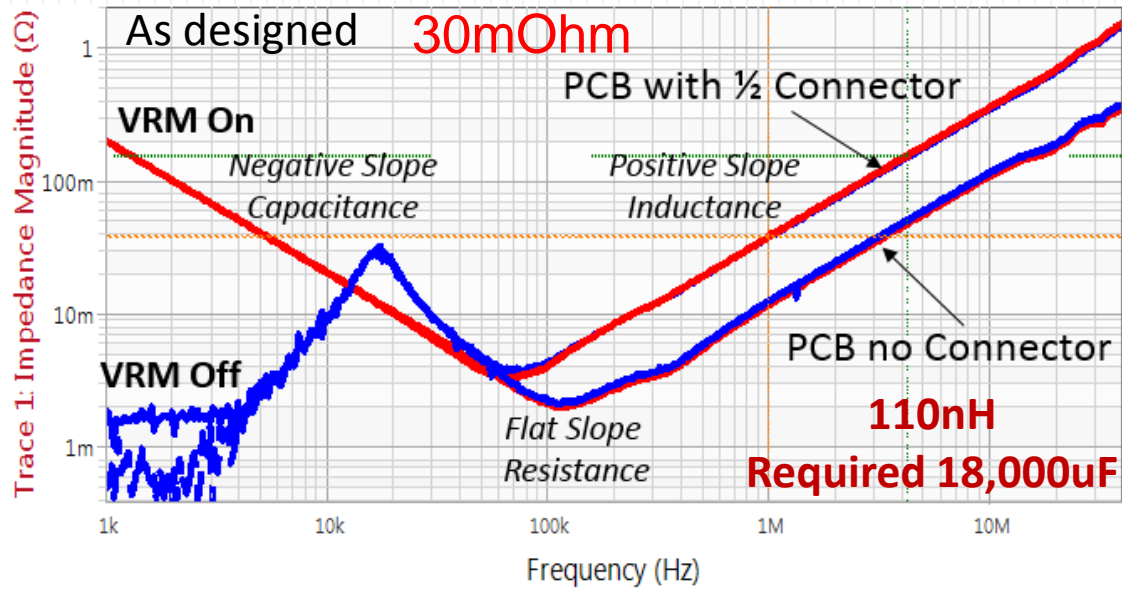Example: Power to 32Gb/s SERDES Transceiver



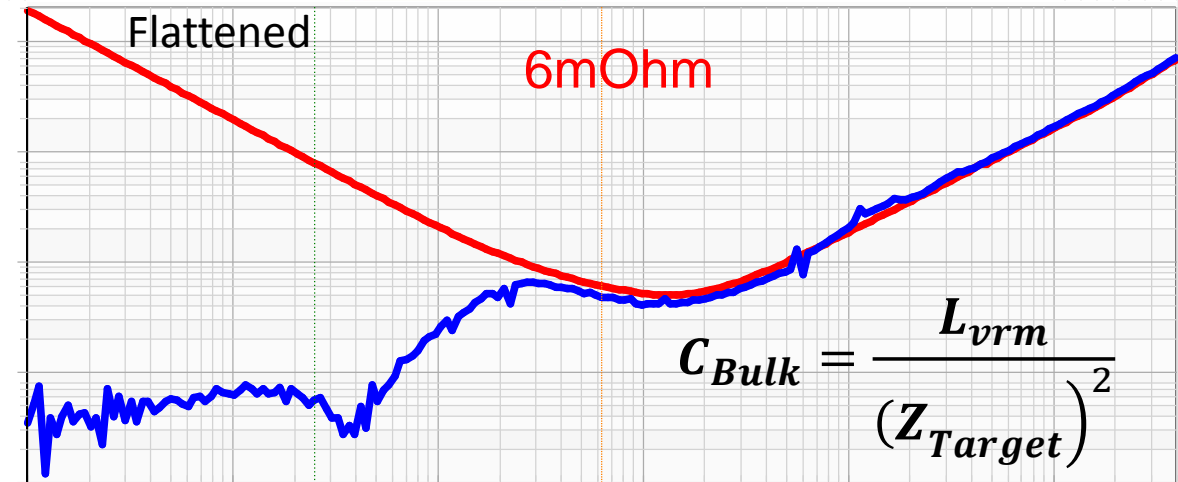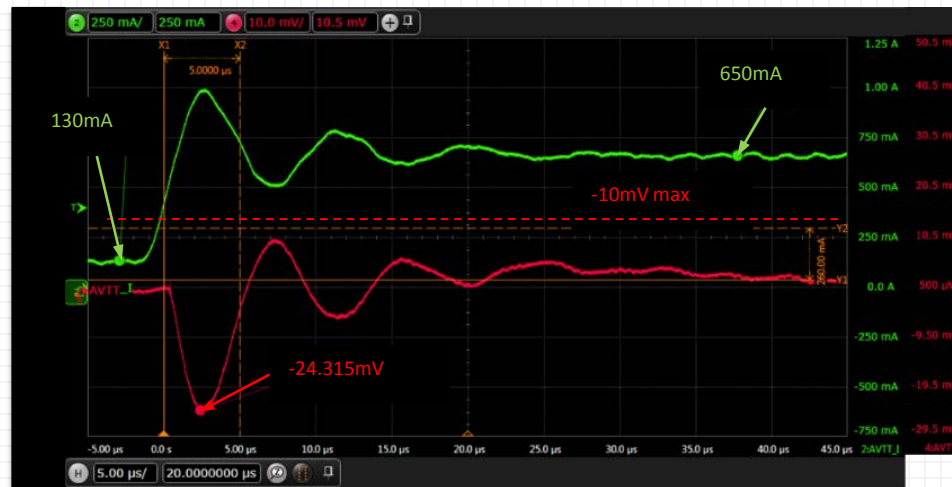This "REFERENCE DESIGN" resulted in exceeding the allowed voltage deviation by 150% when powering just ONE of FIVE transceivers







Example: Power to 32Gb/s SERDES Transceiver

The 1.2V MGTVCC powers the transceivers. There are 10 total transceivers and each results in a 500mA step at turn on. At least one bank of 5 is required or 2.5amps, meaning that the Z_o has to be $< 4m\Omega$ (2.5m Ω in order to account for WC)

The specialized D2Cap™ VRM controller has no compensation or linear control **NO WAY TO FIX IT!**


Measuring the excess inductance and solving for the capacitance requires **18,000uF** to achieve the 10mV allowed transient.

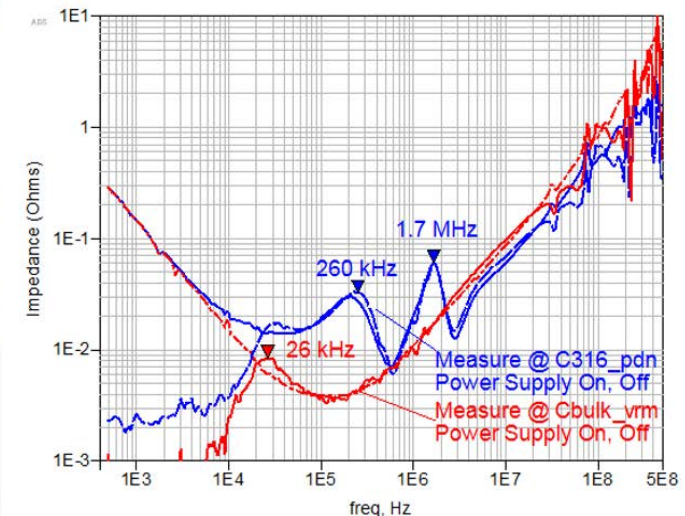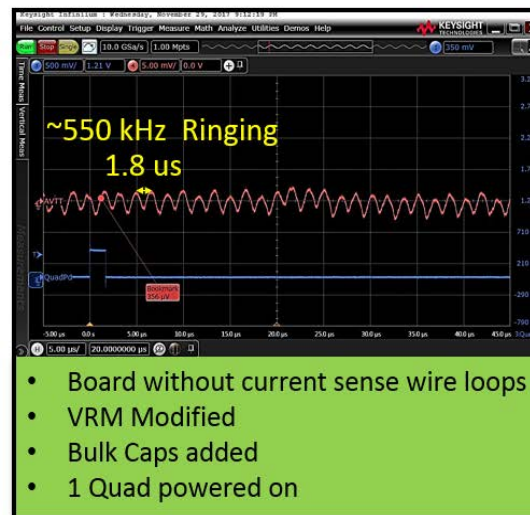  The switching frequency and output inductor were modified at the expense of efficiency. This reduced the required capacitance to 1200uF. **Note: due to 8nH inductance of the pins an additional 1300uF per pin we required after the connector.**



Example: Power Impact Clock Jitter

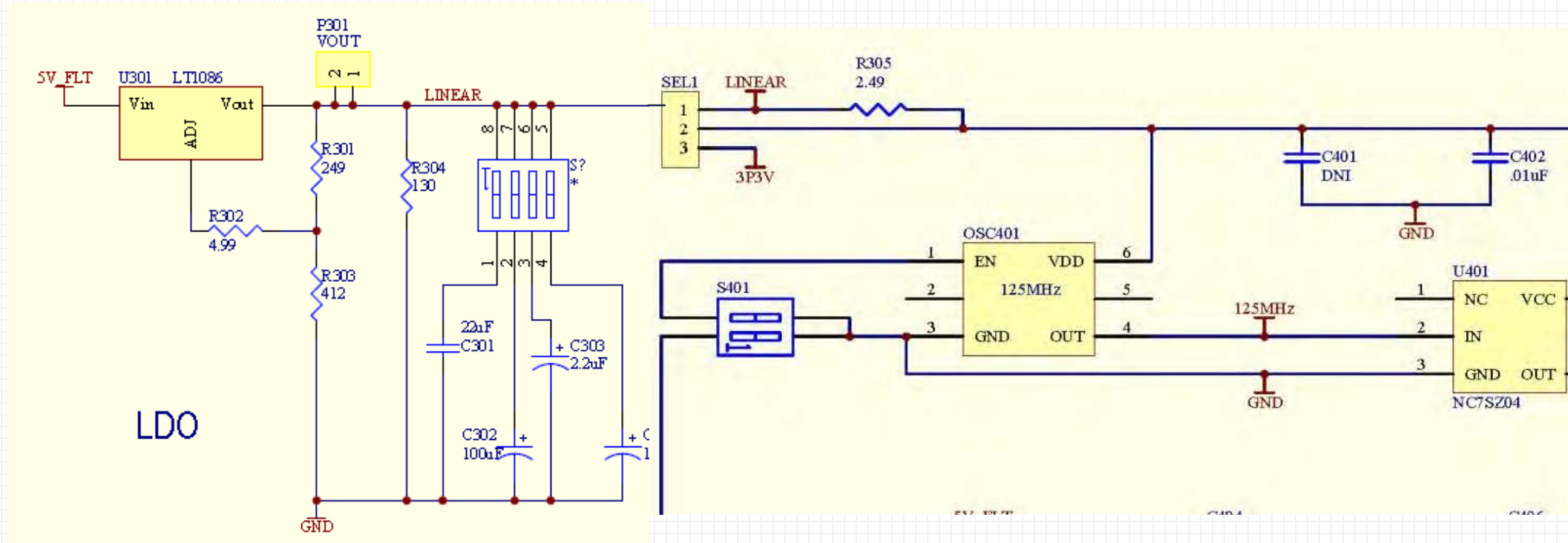3.3V LDO various bulk capacitors
& 10nF Decoupling Cap




Example: Power Impact Clock Jitter

Injecting the Harmonic Comb signal at the Clock capacitor shown earlier reveals the impedance resonance




Clock and buffer

 




10nF cap

Clock output

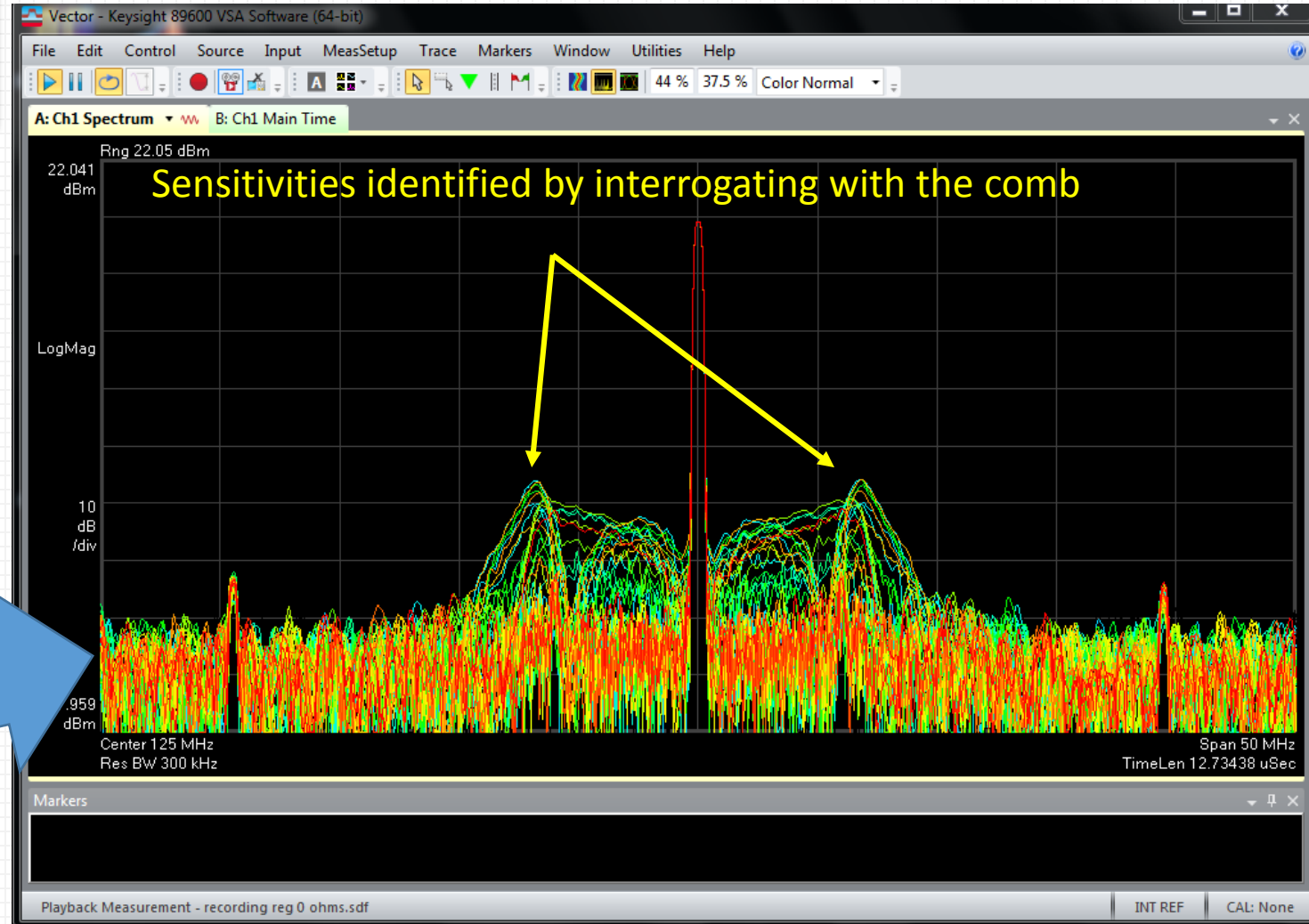

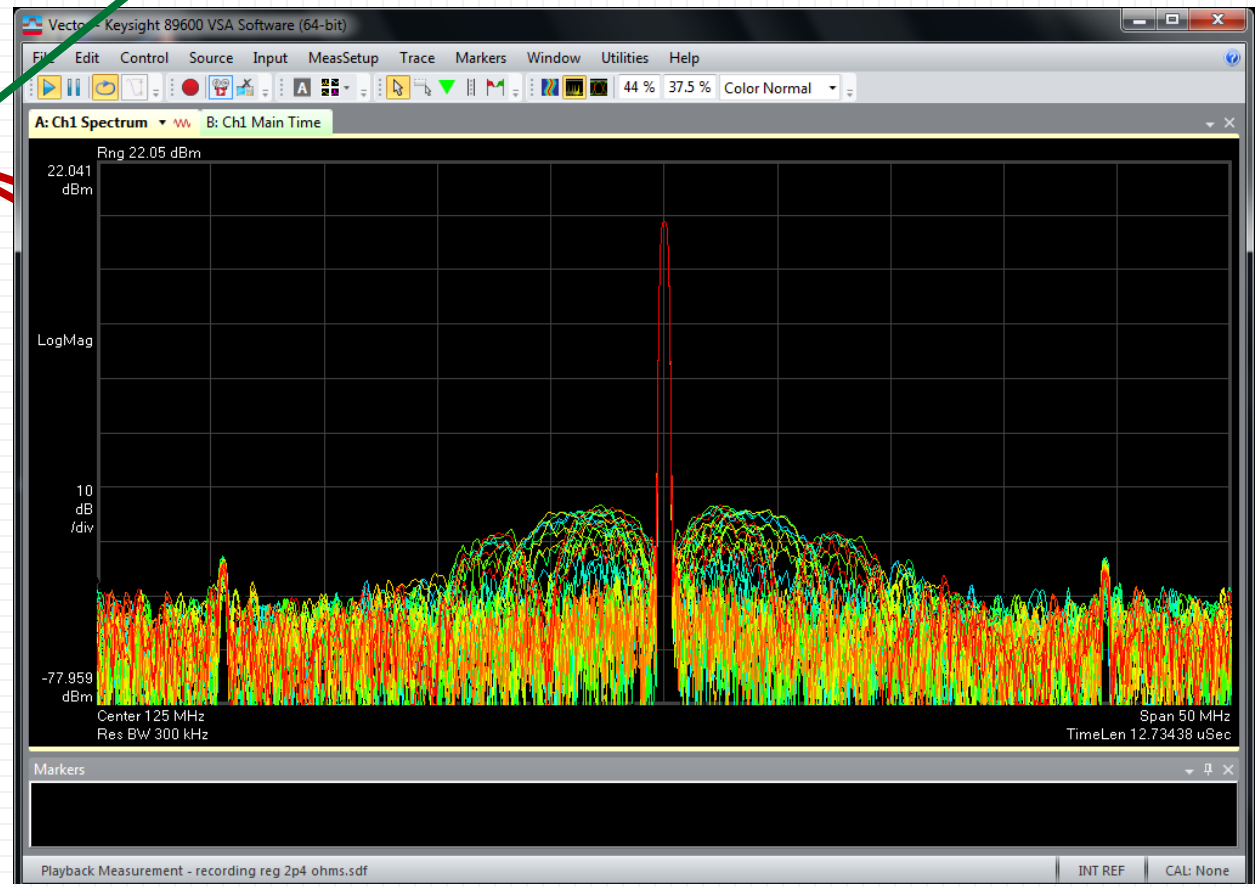 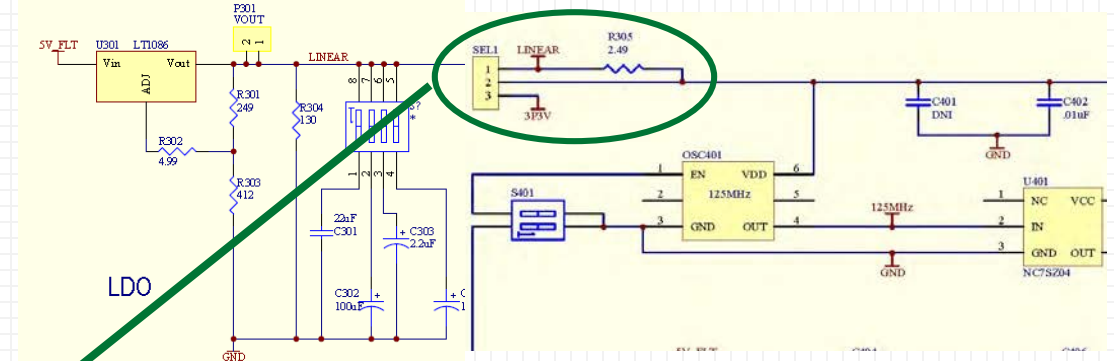Example: Power Impact Clock Jitter

Flattening the impedance eliminates the jitter



YOU CAN'T TEST YOUR WAY OUT OF PI!!

- **PCB design / decoupling “rules-of-thumb” generally don’t work well**
 - ❖ Involves trade-offs - the impact on resonances need to be weighed carefully
 - ❖ Should be based on Test Data
 - ❖ But measurements are often hard to perform – Lack of Access
- **A mismatched VRM exacerbates resonances**
 - ❖ Almost impossible to fix due to lack of controller ESR caps and board space
- **Tolerances make Qs much worse – give rise to rogue waves**
- **Simulation is challenging, time-consuming, and expensive**

Lessons Learned

- **Power Integrity Matters to the Entire System**
 - ❖ Don't ignore it, believe its trivial or irrelevant, or leave it until the end
- **Perform Measurements Prior to Selecting the VRM**
 - ❖ Select the RIGHT VRM, not the BEST VRM
- **Design for Flat Target Impedance**
- **Plan for Iterations/Board Spins *“Get it right the 2nd time”***

References and Resources

1. **Ultra-Low Impedance Measurements Using 2-Port Measurements**
<http://literature.cdn.keysight.com/litweb/pdf/5989-5935EN.pdf>
 2. **PCB Characteristics Affect PDN Performance,**
<http://www.edn.com/design/pc-board/4429719/PCB-characteristics-affect-PDN-performance>
 3. **The Inductive Nature of Voltage Control Loops,**
<https://www.edn.com/electronics-blogs/impedance-measurement-rescues/4438578/The-inductive-nature-of-voltage-control-loops>
 4. **A 5-V Input, 1.6-A Output, Non-Synchronous Buck Converter**
<http://www.ti.com/lit/ug/slvu153/slvu153.pdf>
 5. **Power Integrity For 32 Gb/S Serdes Transceivers, Heidi Barnes, Jack Carrel, Steve Sandler, Designcon 2018**
<http://schedule.designcon.com/session/power-integrity-for-32-gbs-serdes-transceivers/851162>
 6. **Top Three EMI and Power Integrity Problems with On-Board DC-DC Converters and LDO Regulators**
<https://interferencetechnology.com/top-three-emi-power-integrity-problems-board-dc-dc-converters-ldo-regulators/#>
- **AEi Systems Power Integrity Publications**
 - ❖ https://www.aeng.com/power_integrity.htm
 - **How to Design for Power Integrity YouTube Video Series**
 - ❖ <https://www.youtube.com/playlist?list=PLtq84kH8xZ9FNXAsf-odoGNe6h5A6D3in>
 - **SI & PI Resources from Keysight EEs of EDA**
 - ❖ <https://www.keysight.com/main/editorial.jsp?cc=US&lc=eng&ckey=2658533&nid=-11143.0.00&id=2658533>
 - **Power Integrity Book: Measuring, Optimizing, and Troubleshooting Power Related Parameters in Electronics Systems**